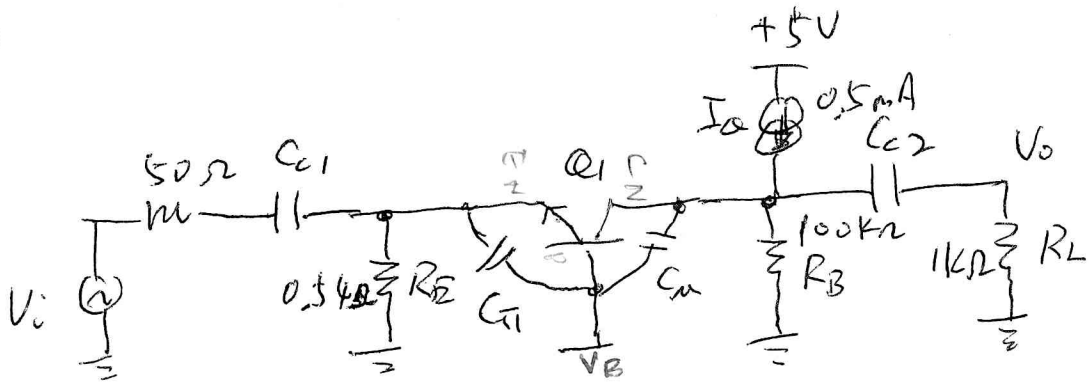



(1)



Given: $\beta = 100$
 $V_A \rightarrow \infty$
 $C_{\mu} = 1 \text{ pF}$
 $f_c = 285 \text{ MHz}$
 $V_T = 25 \text{ mV}$

Find: WH

Step 1: Q point calculations

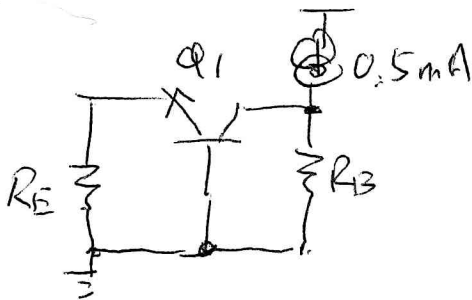

$I_C \approx 0.5 \text{ mA}$


$g_m = \frac{I_C}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 0.02 \text{ S}$

$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.02 \text{ S}} = 5 \text{ k}\Omega$

Since $V_A = \infty$, $r_o = \infty$

Step 2: Draw high frequency small-signal equivalent circuit.

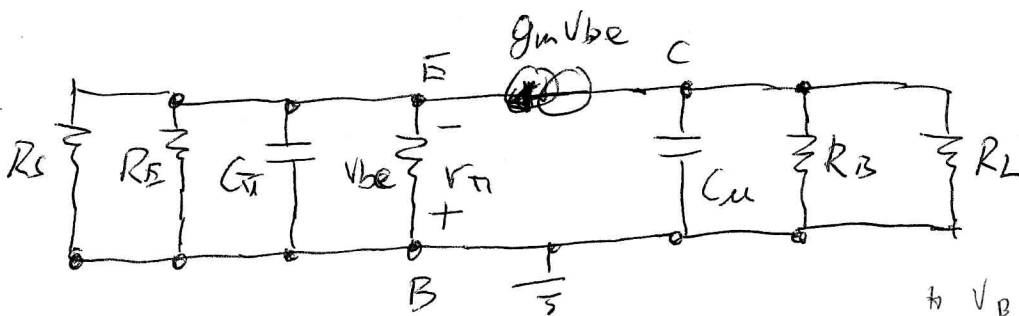
- standard AC equivalent
- (i) Coupling capacitors $C_{c1}, C_{c2} \rightarrow$ short circuit
 - (ii) DC voltage source $V_{CC} = 5 \text{ V} \rightarrow$ short circuit



Note that you cannot remove C_{π} & C_{μ} .

$V_B \rightarrow$ gnd for AC circuit.

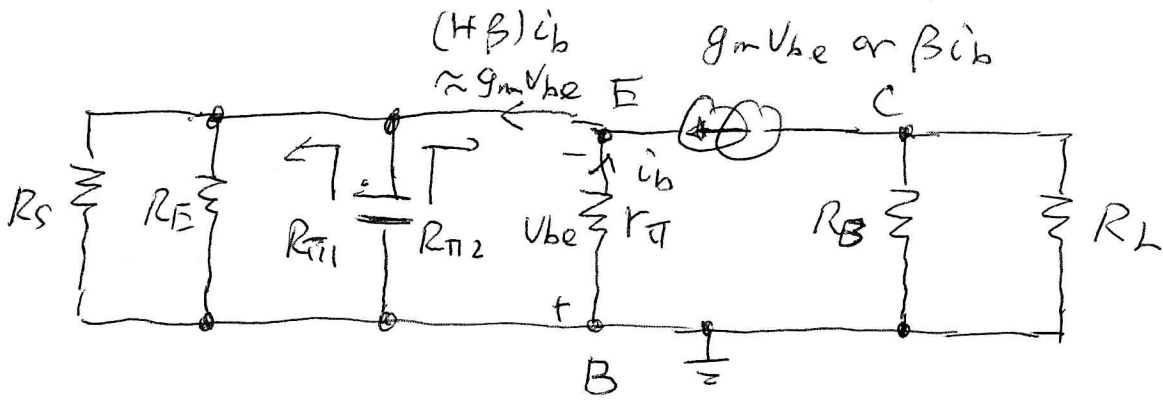Step 3: Open circuit C_u and find $R_{\pi 0}$ seen by C_{π}




$$R_{\pi 1} = R_s \parallel R_E$$

$$R_{\pi 2} = \frac{r_{\pi}}{\beta + 1} \text{ or } R_{\pi} \approx \frac{v_{be}}{g_m v_{be}} = \frac{1}{g_m}$$

$$R_{\pi 0} = R_{\pi 1} \parallel R_{\pi 2} = R_s \parallel R_E \parallel \frac{r_{\pi}}{\beta + 1} = 50 \parallel 500 \parallel \frac{5000}{101} = 24 \Omega$$

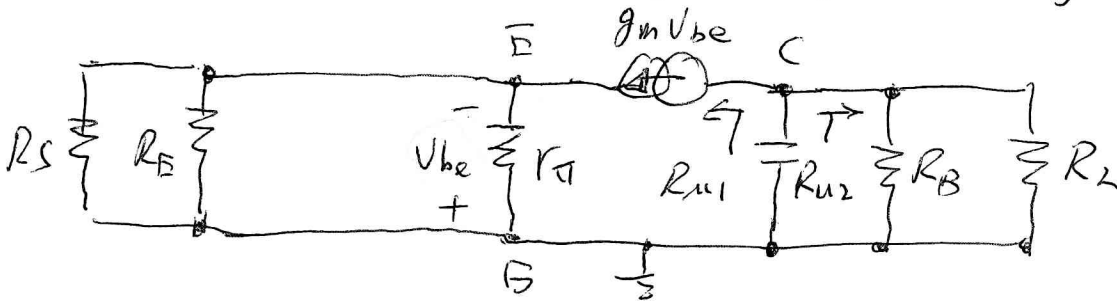Open circuit C_{π} and find R_{u0} seen by C_u



$$v_{be} = 0 \Rightarrow g_m v_{be} (R_s \parallel R_E \parallel r_{\pi}) \Rightarrow v_{be} + g_m v_{be} (R_s \parallel R_E \parallel r_{\pi}) = 0$$

$$v_{be} \cdot [1 + g_m (R_s \parallel R_E \parallel r_{\pi})] = 0$$

Since $1 + g_m (R_s \parallel R_E \parallel r_{\pi}) \neq 0$, $v_{be} = 0$


$$\Rightarrow g_m v_{be} = 0, \text{ Hence, } R_{u1} = \infty$$

$$R_{u2} = R_B \parallel R_L = 100 \text{ k}\Omega \parallel 1 \text{ k}\Omega = 990 \Omega, \quad R_{u0} = R_{u1} \parallel R_{u2} = 990 \Omega$$

By OCTC method, $\omega_H = \frac{1}{R_{\pi 0} C_{\pi} + R_{u0} C_u}$

$$\omega_H = \frac{1}{24 \times 10^{-12} + 990 \times 10^{-12}} = \underline{\underline{813 \text{ rad/s}}}$$

(2)

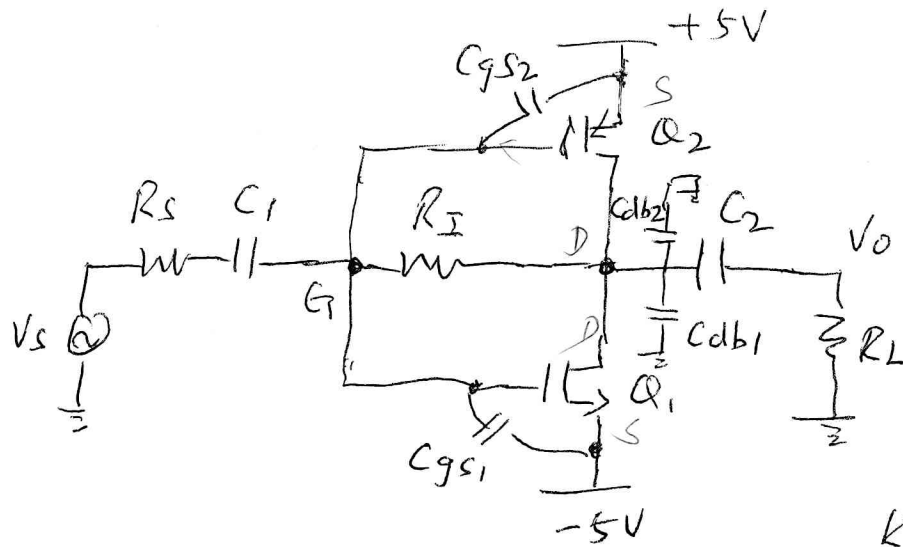

Find ω_L
 Given: $R_S = 1k\Omega$
 $C_1 = 1\mu F$
 $C_2 = 1nF$
 $R_I = 5M\Omega$
 $R_L = 10k\Omega$

$$K_n = K_p = 50 \mu A/V^2$$

$$V_{TN} = |V_{TP}| = 2V$$

$$\lambda = 0.005 V^{-1}$$

Step 1: Find the biasing point

$$V_{SG2} + V_{GS1} = 10V \Rightarrow V_{GS} = 5V$$

$$I_{D1} = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) \approx \frac{K_n}{2} (V_{GS} - V_{TN})^2 = \frac{50 \mu A/V^2}{2} (5V - 2V)^2$$


$$g_{m1} = g_{m2} = g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} \approx \sqrt{2K_n I_D} = \sqrt{2 \times 50 \mu A/V^2 \times 225 \mu A} = 225 \mu A$$


$$r_{o1} = r_{o2} = r_o = \frac{1}{\lambda I_D} = 0.888 M\Omega = 150 \mu A/V$$

Step 2: Draw low-frequency small-signal equivalent circuit.


Remove parasitic caps: C_{gs1} , C_{gs2} , C_{db1} , C_{db2}

Keep C_1 and C_2

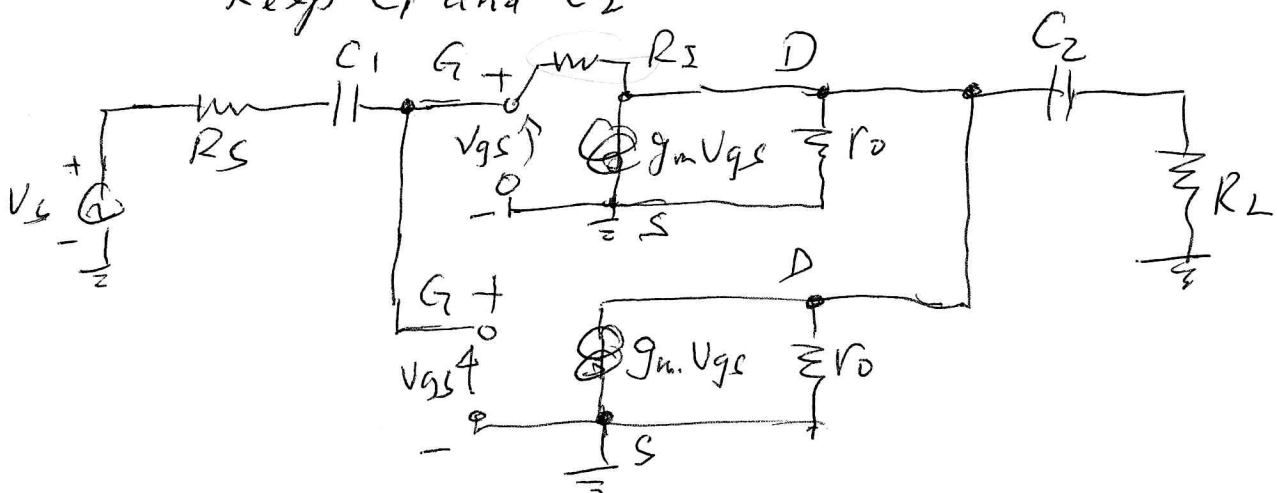

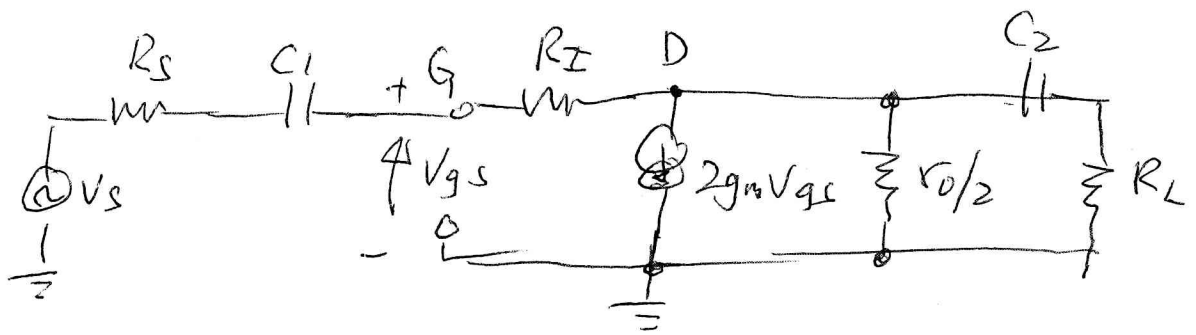

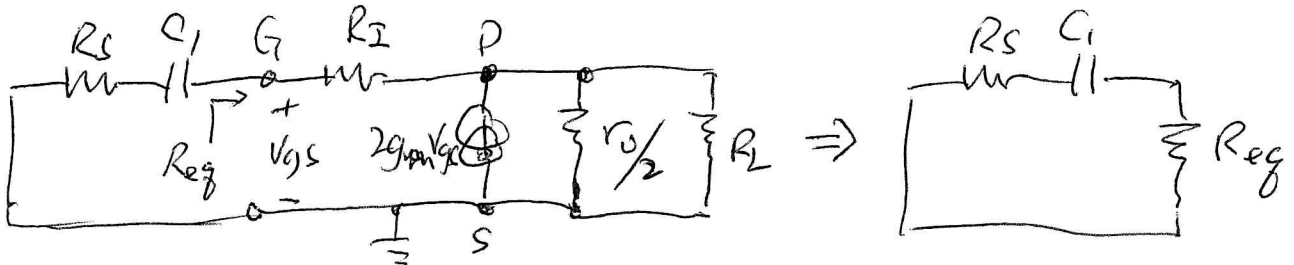Step 3: Find R_{1s} seen by C_1 by shorting other capacitors



$$\frac{V_g - V_d}{R_I} = 2g_m V_g + \frac{V_d}{r_o/2} + \frac{V_d}{R_L} \Rightarrow \left(\frac{1}{R_I} - 2g_m\right) V_g = \left(\frac{2}{r_o} + \frac{1}{R_L} + \frac{1}{R_I}\right) V_d$$


For $r_o = 0.888 \text{ M}\Omega$, $R_L = 10 \text{ k}\Omega$, $R_I = 5 \text{ M}\Omega$, $g_m = 150 \mu\text{A/V}$,

we get $V_d = -2.94 V_g$, $R_{eq} = \frac{V_g}{\frac{V_g - V_d}{R_I}} = \frac{V_g R_I}{V_g + 2.94 V_g}$

$$\therefore R_{1s} = R_{eq} + R_S = 1.27 \text{ M}\Omega + 1 \text{ M}\Omega = 2.27 \text{ M}\Omega$$

$$= \frac{5 \text{ M}\Omega}{3.94} = 1.27 \text{ M}\Omega$$

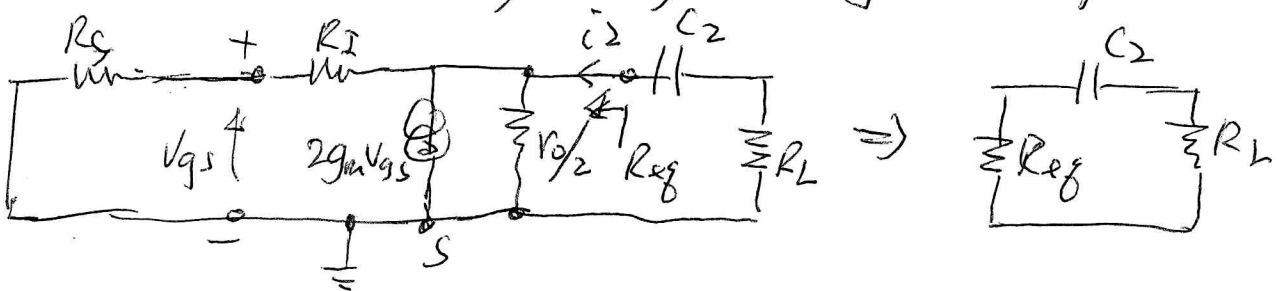Find R_{2s} seen by C_2 by shorting other capacitors



$$i_2 = 2g_m V_g + \frac{V_d}{r_o/2} + \frac{V_d - V_g}{R_I} \Rightarrow R_{eq} = \frac{V_d}{i_2} = \frac{V_d}{2g_m V_g + \frac{2V_d}{r_o} + \frac{V_d - V_g}{R_I}}$$

$$\therefore V_g = \frac{R_S}{R_S + R_I} \cdot V_d = \frac{1 \text{ M}\Omega}{1 \text{ M}\Omega + 5 \text{ M}\Omega} V_d = 0.167 V_d = 6 V_g = V_d$$

$$\therefore R_{eq} = \frac{6 V_g}{\left(2 \times 150 \mu\text{A/V} \times V_g + \frac{12 V_g}{0.888 \text{ M}\Omega} + \frac{1 V_g}{5 \text{ M}\Omega}\right)}$$

$$R_{2s} = R_{eq} + R_L = 19.08 \text{ k}\Omega + 10 \text{ k}\Omega = 29.08 \text{ k}\Omega, \text{ By SCTC method}$$

$$\omega_L = \sum_{i=1}^n \frac{1}{R_i C_i} \Rightarrow \omega_L = \frac{1}{2.27 \text{ M}\Omega \times 1 \mu\text{s}} + \frac{1}{29.08 \text{ k}\Omega \times 1 \mu\text{s}} = \underline{\underline{34.9 \text{ rad/s}}}$$