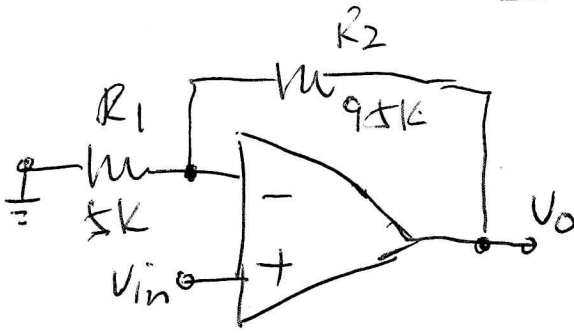


1(a)

(i)



$$\beta = \frac{R_1}{R_1 + R_2} = \frac{5}{5 + 95}$$


$$= 0.05$$

$$A_{CL} = \frac{1}{\beta} = 20$$

$$A_{CL} \cdot BW_{CL} = 1 \cdot f_t$$

$$\therefore BW_{CL} = \frac{f_t}{A_{CL}} = \beta \cdot f_t = \underline{\underline{60 \text{ kHz}}}$$

(ii)

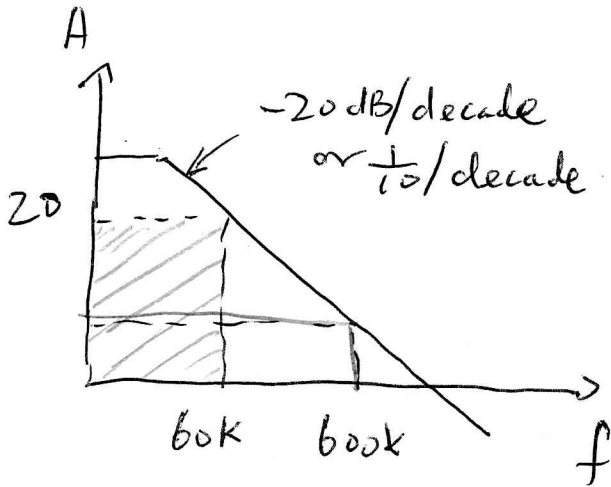


$$20 \times 60k = 600k \times A_{CL}(600k)$$

$$\therefore A_{CL}(600k) = \frac{1200k}{600k}$$

$$= \underline{\underline{2V/V}}$$

1(b)

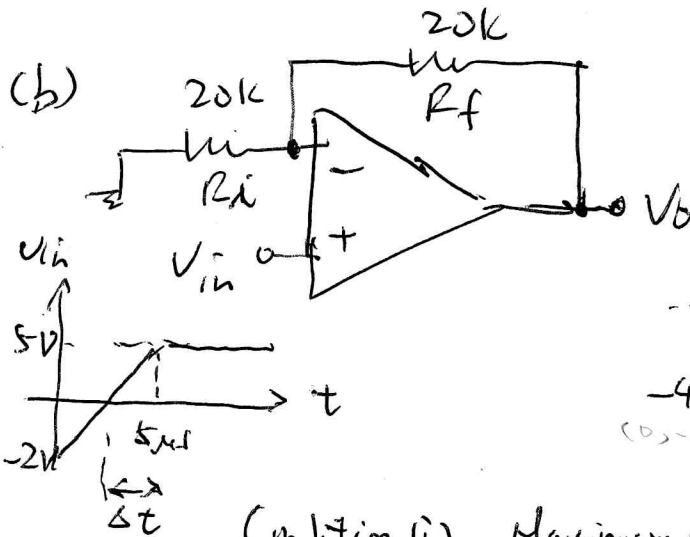

$$A_{CL} = 1 + \frac{R_f}{R_i} = 1 + \frac{20k}{20k}$$

$$= 2$$

$$\frac{14mV}{5} = 2.8$$


Condition (i), Maximum Response Time with given SR

$$t_{max} = \frac{14V}{SR} = \frac{14V}{4V/\mu s} = 3.5 \mu s < \Delta t = 5 \mu s$$

Condition (ii), BW response time of Amplifier

$$t_r = 0.35 / BW_{CL} = \frac{0.35}{\beta \cdot f_t} = \frac{0.35}{0.05 \times 2MHz} = 0.35 \mu s \ll \Delta t \text{ (5μs)}$$

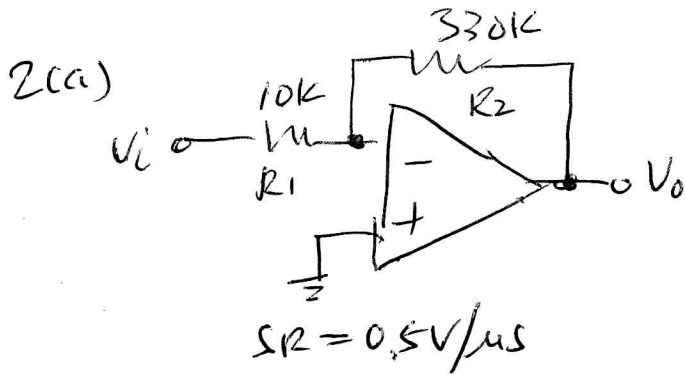Condition (i) & (ii)  $\Rightarrow$  no distortion.



$$A_{CL} = -\frac{R_2}{R_1} = -\frac{330k}{10k} = -33V/V$$

$$V_o = V_p A_{CL} \sin \omega t$$

$$\frac{dV_o}{dt} = V_p A_{CL} \omega \cos \omega t \leq SR$$

$$\omega_{max} = \frac{SR}{V_p \cdot A_{CL}}$$

Input Signal	$\omega$ (rad/s)	$V_p$ (V)	$\omega_{max}$ (rad/s)	$\omega < \omega_{max}$
$V_1$	$10^6$	0.01	$1.515 \times 10^6$	Yes
$V_2$	$350 \times 10^3$	0.05	$303.03 \times 10^3$	No $\rightarrow$ SR distortion
$V_3$	$200 \times 10^3$	0.1	$151.5 \times 10^3$	No $\rightarrow$ SR distortion
$V_4$	$50 \times 10^3$	0.2	$75.75 \times 10^3$	Yes

2(b) For fixed  $V_p$ , two remedies

(i) Find an op-amp with greater SR

(ii) Reduce the  $A_{CL}$  of op-amp.

Consider case (i)  $\frac{SR}{0.05 \times 33} \geq 350 \times 10^3 \Rightarrow SR \geq 577.5 \times 10^3 V/\mu s$

For  $V_2$ :


For  $V_3$ :  $\frac{SR}{0.1 \times 33} \geq 200 \times 10^3 \Rightarrow SR \geq 660 \times 10^3 V/\mu s$

Consider case (ii)  $\frac{0.5 \times 10^6}{0.05 \times A_{CL}} \geq 350 \times 10^3 \Rightarrow A_{CL} \leq$

For  $V_2$ :


For  $V_3$ :  $\frac{0.5 \times 10^6}{0.1 \times A_{CL}} \geq 200 \times 10^3 \Rightarrow A_{CL} \leq$

3(a)

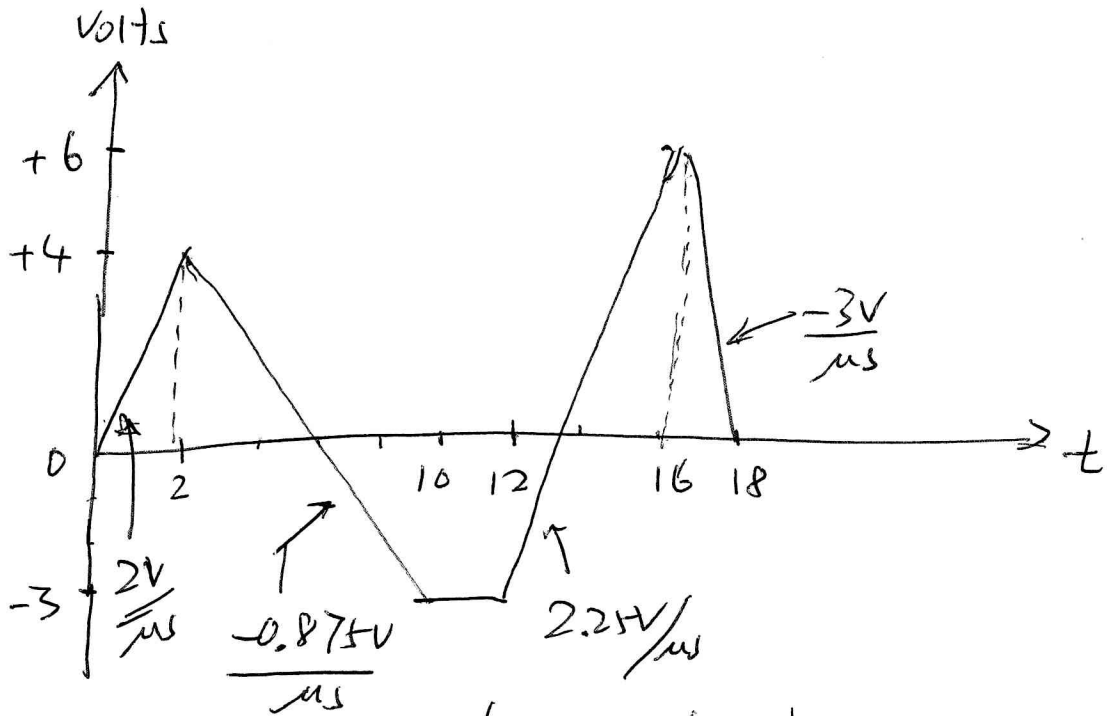

$$\text{Worst case } SR = |SR_{max}| = \left| \frac{\Delta V}{\Delta t} \right| = \underline{\underline{3V/\mu s}}$$

3(b)

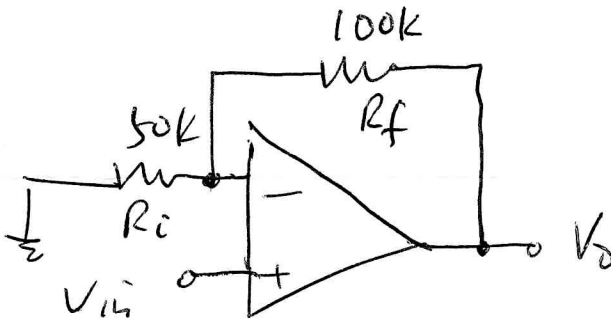


$$ACL = 1 + \frac{R_f}{R_i} = 1 + \frac{100k}{50k} = 3V/V$$

$$\therefore \text{input slope} = 3V/\mu s,$$

$$\therefore \text{output slope} = 3 \times 3V/\mu s = 9V/\mu s$$

4 (i) Using Inverting Configuration

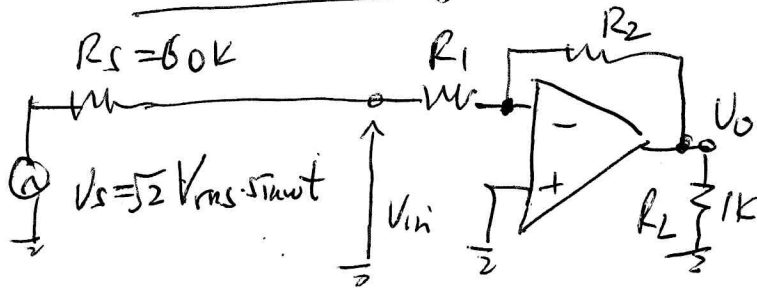

Choose  $R_1 = 47k$

$$V_{in} = V_s \times \frac{R_1}{R_1 + R_s} = 1 \times \frac{47k}{47k + 60k}$$


$$= 0.44 V_{rms}$$

For  $V_o = 2.5 V_{rms}$ ,  $A_{CL} = \frac{V_o}{V_{in}} = \frac{2.5 V_{rms}}{0.44 V_{rms}} = 5.68 V/V$

$\therefore R_2 = A_{CL} \cdot R_1 = 5.68 \times 47k = 267k$

Use  $R_2 = \underline{270k}$

(ii) Using Non-Inverting Configuration

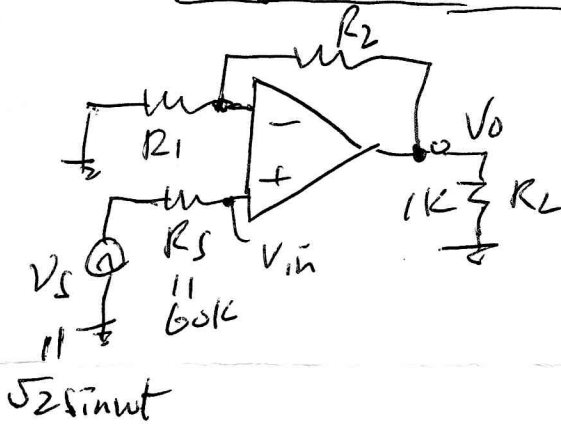


$$A_{CL} = \frac{V_o}{V_{in}} = \frac{V_o}{V_s} = \frac{2.5V}{1V} = 2.5 V/V$$

$$1 + \frac{R_2}{R_1} = 2.5 \Rightarrow \frac{R_2}{R_1} = 1.5$$

Choose  $R_2 = \underline{150k}$

$\& R_1 = \frac{150k}{1.5} = \underline{100k}$

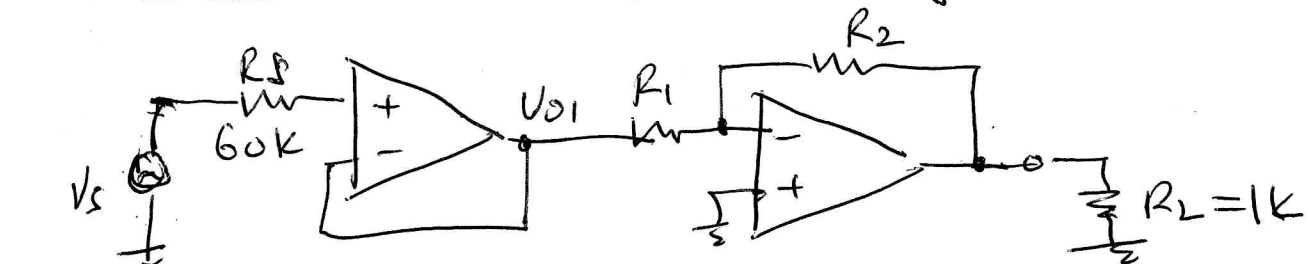(iii) Using a Voltage Follower plus Inverting Amplifier



$$\frac{V_o}{V_{o1}} = \frac{V_o}{V_s} = \frac{-2.5V}{1V} = -2.5 V/V$$

$\therefore \frac{R_2}{R_1} = 2.5 \Rightarrow R_2 = 2.5 R_1$

Choose  $R_1 = \underline{47k}$ ,  $R_2 = 117.5k$

Use  $R_2 = \underline{120k}$